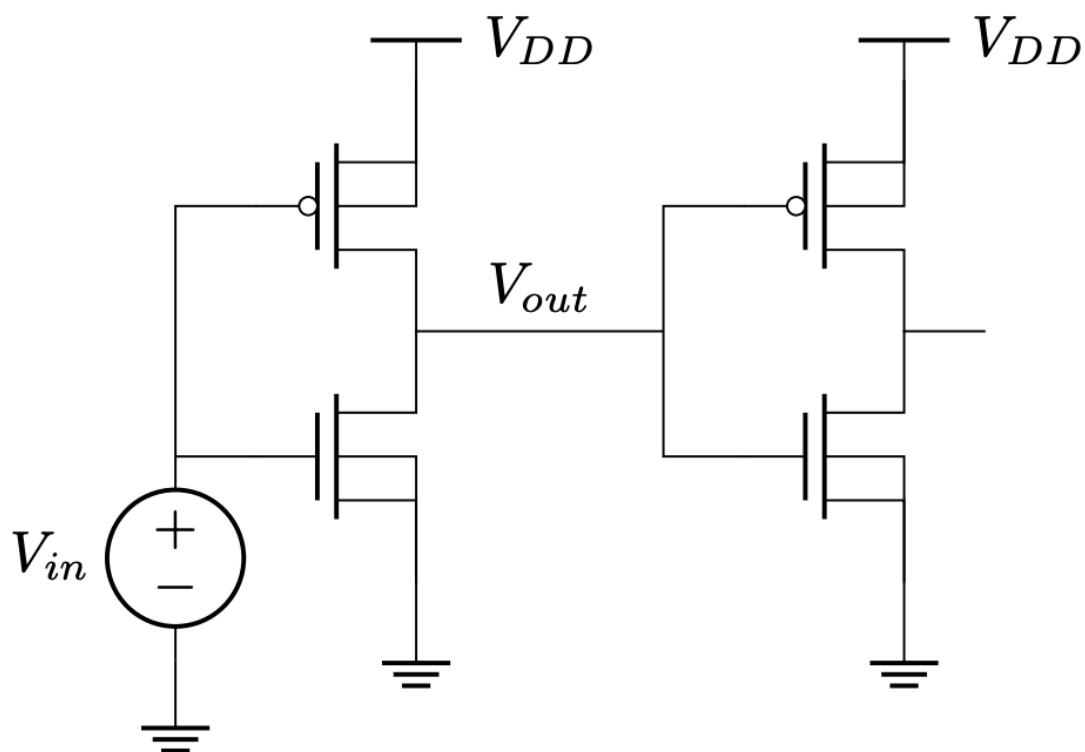


# EE5311 Tutorial 3 Report - EE22B070

Himanshu R. Borkar

13/02/2025

## Problem Schematic:




**Pulse Specifications:** 0 to  $V_{DD}$  with rise and fall time of 5 ps and pulse width of 250 ps.


### 1.(a)

Set  $V_{DD} = 1.8V$ . Assume that  $L_n = L_p = 0.15 \mu m$  and  $W_n = 0.42 \mu m$ . Obtain the delay for  $W_p = 0.42 \mu m, 0.84 \mu m, 1.26 \mu m$ .


## Schematic:

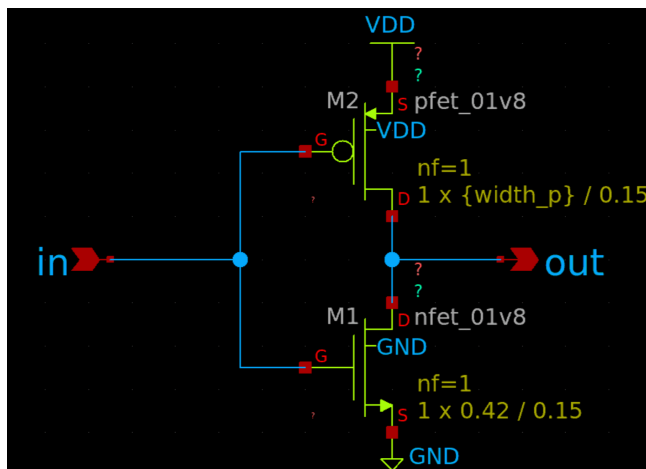

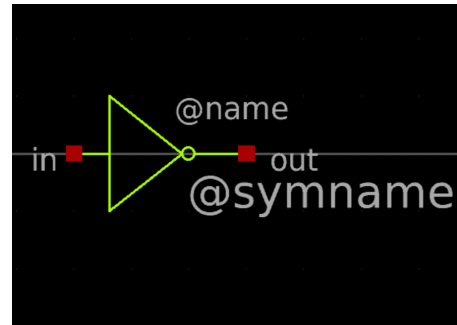Schematic: inverter with parameterized pMOS width



Symbol for inverter given on the left

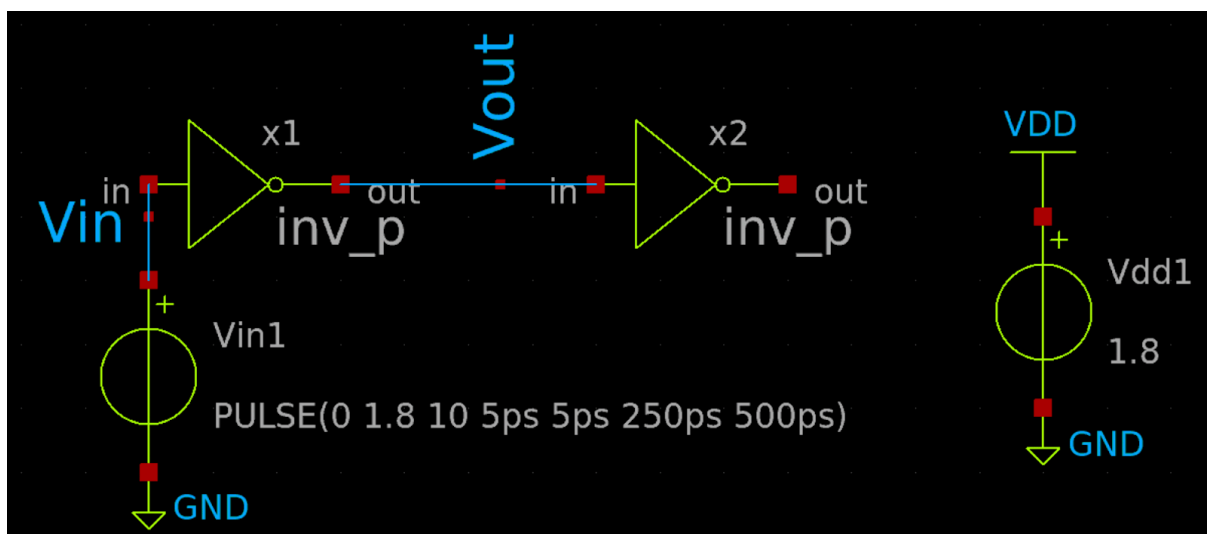


Schematic for 1(a)

## Sim-Code:

```
.param width_p = 0.42
.control
foreach wp 0.42 0.84 1.26
  alterparam width_p = $wp
  reset
  tran 0.1p 500p
  plot v(Vout) v(Vin) title "pMOS width = $wp"
  meas tran thl trig v(Vin) val = 0.9 rise = 1 targ v(Vout) val = 0.9 fall = 1
  meas tran tlh trig v(Vin) val = 0.9 fall = 1 targ v(Vout) val = 0.9 rise = 1
  let delay = ($&thl + $&tlh)/2
  echo w : $wp delay : $&delay
end
.endc
```

## Measurements:

- For  $W_p = 0.42 \mu\text{m}$

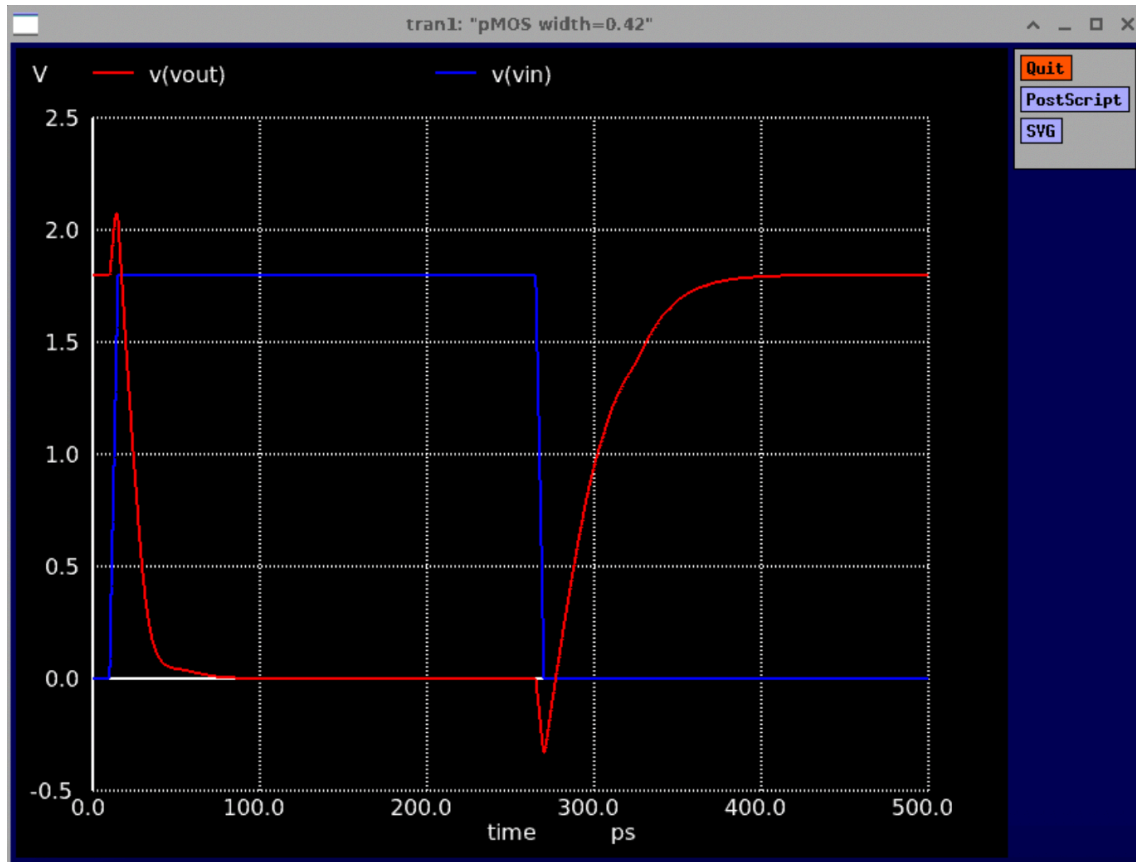

$V_{in}$  (pulse) vs  $V_{out}$

- There are noticeable spikes at the rising and falling edges due to the charging and discharging of the junction and sw cap between the drain and gate.

### Initial Transient Solution


Node	Voltage
vin	0
vdd	1.8
vout	1.8
net1	4.53092e-08
vdd1#branch	-1.81498e-11
vin1#branch	0

Reference value : 3.55950e-10  
No. of Data Rows : 5020  
thl = 1.277011e-11 targ= 2.527011e-11 trig= 1.250000e-11  
tlh = 3.088892e-11 targ= 2.983889e-10 trig= 2.675000e-10  
w : 0.42 delay : 2.18295E-11

- Final Ans:** The delay for  $W_p = 0.42 \mu\text{m}$  is **21.82 ps**.

$$T_{\text{rise}} = 30.88 \text{ ps}, T_{\text{fall}} = 12.77 \text{ ps}$$

- For  $W_p = 0.84 \mu\text{m}$ :

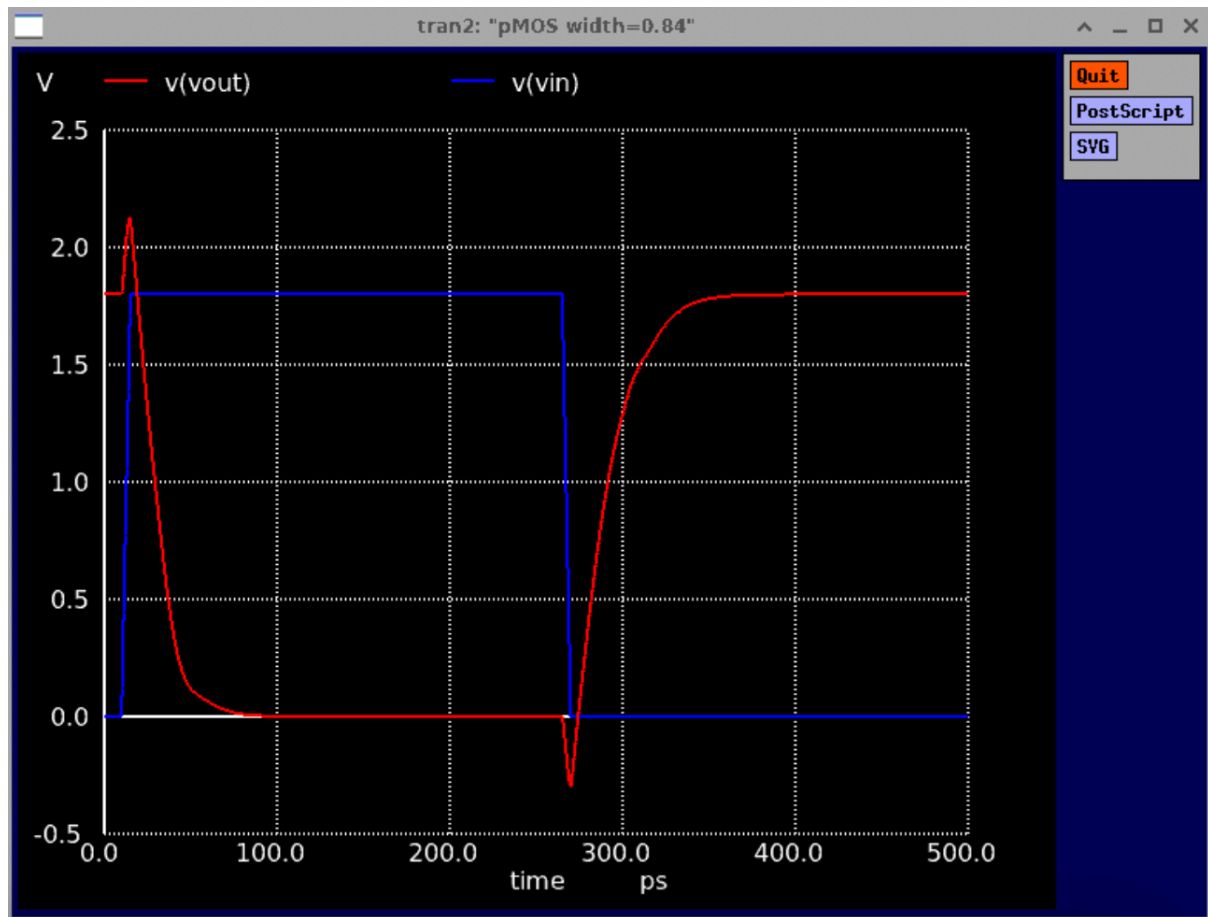

$V_{in}$  (pulse) vs  $V_{out}$

- Spikes are similar to the  $0.42 \mu\text{m}$  case.

Initial Transient Solution


Node	Voltage
vin	0
vdd	1.8
vout	1.8
net1	6.71229e-07
vdd1#branch	-2.43518e-10
vin1#branch	0

Reference value : 1.49250e-10  
 No. of Data Rows : 5020  
 thl = 1.822964e-11 targ= 3.072964e-11 trig= 1.250000e-11  
 tlh = 2.168397e-11 targ= 2.891840e-10 trig= 2.675000e-10  
 w : 0.84 delay : 1.99568E-11

- Final Ans:** The delay for  $W_p = 0.84 \mu\text{m}$  is **19.95 ps**.

$$T_{\text{rise}} = 21.68 \text{ ps}, T_{\text{fall}} = 18.23 \text{ ps}$$

- For  $W_p = 1.26 \mu\text{m}$ :

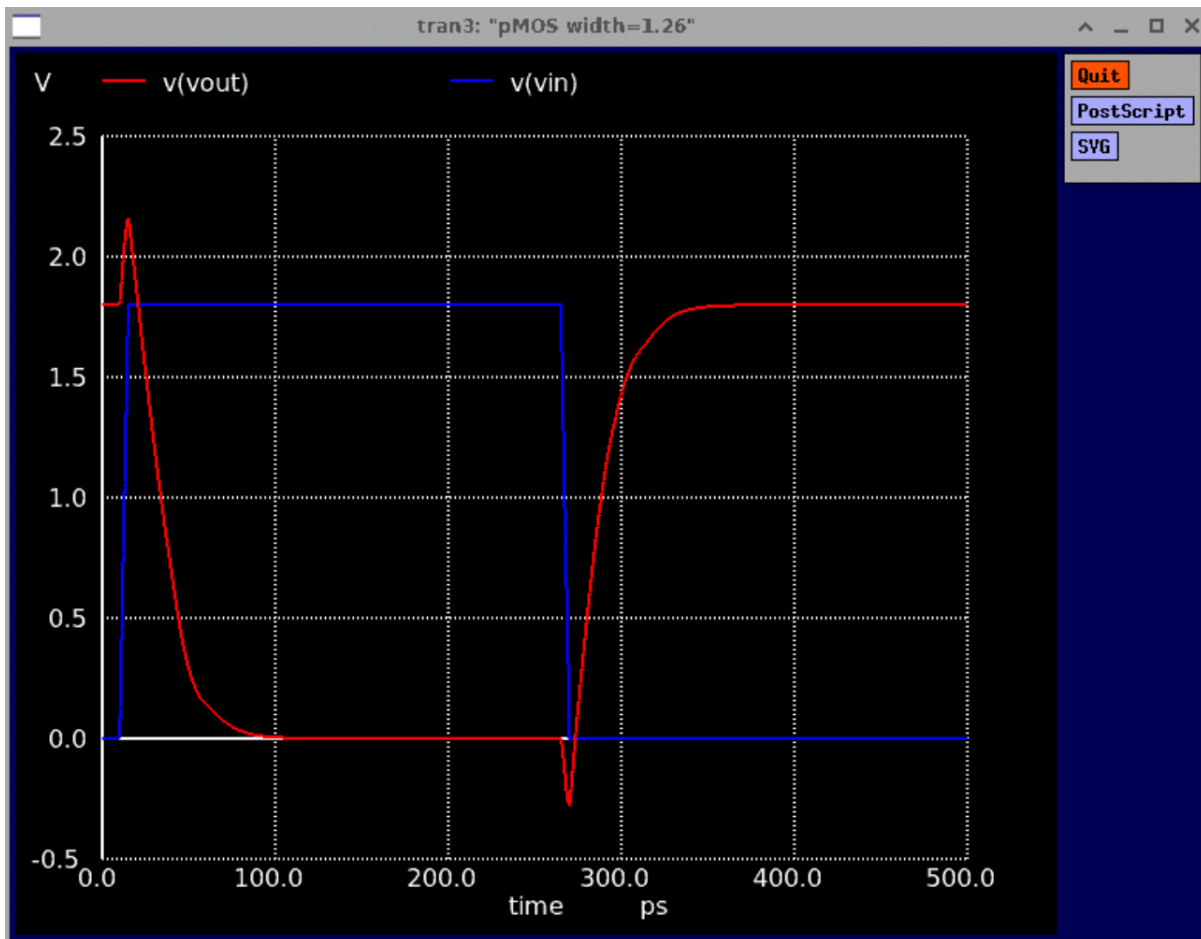

$V_{in}$  (pulse) vs  $V_{out}$

- Spikes are similar to the  $0.42 \mu\text{m}$  and  $0.84 \mu\text{m}$  cases.

#### Initial Transient Solution

Node	Voltage
-----	-----
vin	0
vdd	1.8
vout	1.8
net1	9.60947e-07
vdd1#branch	-3.47833e-10
vin1#branch	0

Reference value : 3.57050e-10

No. of Data Rows : 5020

thl = 2.327333e-11 targ= 3.577333e-11 trig= 1.250000e-11

tlh = 1.898207e-11 targ= 2.864821e-10 trig= 2.675000e-10

w : 1.26 delay : 2.11277E-11

- **Final Ans:** The delay for  $W_p = 1.26 \mu\text{m}$  is **21.12 ps**

$$T_{\text{rise}} = 18.98 \text{ ps}, T_{\text{fall}} = 23.27 \text{ ps}$$

## Inference from Plots:

As we increase the  $W_p$ , the rise time decreases. This is explained by the formula:

$$t_{PLH} \propto C_{Total}/W_p$$

And  $C_{Total}$  is also dependent on  $W_p$ .

And in the case of fall time, there is no  $W_p$  in denominator, hence, the rise time increases.

### 1.(b) & (c)

b) Set  $W_p$  so that the delay is minimized. Plot the delay as a function of  $V_{DD}$  for  $V_{DD} = 1V$  to  $1.8V$  in steps of  $0.1V$ . How does it compare with analytical estimates?

c) Plot the measured and estimated energy-delay product as a function of  $V_{DD}$ . What is the optimum  $V_{DD}$ ?

## Calculations:

1. (b) from (a), we obtained the optimal  $W_p$  value to be  $0.84 \mu m$ . Now we consider the variation of delay w.r.t time.

$$t_{pLH} = \frac{C_{total}(V_{DD}/2) \cdot (E_{cp}L + (V_{DD} - V_{TP}))}{k_p \left(\frac{W}{L}\right)_p E_{cp}L (V_{DD} - V_{TP})^2}$$

for  $W_p = 0.84$

$$t_{pHL} = \frac{C_{total}(V_{DD}/2) \cdot (E_{cn}L + (V_{DD} - V_{TN}))}{k_n \left(\frac{W}{L}\right)_n E_{cn}L (V_{DD} - V_{TN})^2}$$

$$C_{total} = 3.2 \text{ ff}$$

$$t_{pLH} = \frac{C_{total}(V_{DD}/2) \cdot (E_{cp}L + (V_{DD} - V_{TP}))}{k_p \left(\frac{W}{L}\right)_p E_{cp}L (V_{DD} - V_{TP})^2}$$

$$\Rightarrow t_{pLH} = C \frac{(E_{CL} + V_{DD} - |V_{TP}|) V_{DD}}{(V_{DD} - |V_{TP}|)^2}$$

$$\Rightarrow E_{CL} = \frac{2 V_{SAT,P} L_p}{\mu_p} = \frac{2 \times 3 \times 10^4}{0.009} \times 0.15 \mu$$

$$= 100 \times 10^4 \times 10^{-6} = 1 V$$

$$\Rightarrow t_{pLH} = C_1 \left( \frac{1 + 0.3}{0.5^2} \right)$$

$$C_1 = \frac{5.2 \times 10^{-15} \times 10^{-9}}{2 \left( 36.72 \times \left( \frac{0.84}{0.15} \right) \times 1 \right) \mu}$$

$$= 0.00778 \times 10^{-9}$$

$$= 7.78 \times 10^{-12}$$

$$\frac{2 \times 8 \times 10^4}{0.025} \times 0.15 = 0.96$$

$$\therefore t_{pHL} = \frac{C_{total}(V_{DD}/2) \cdot (E_{CL} + (V_{DD} - V_{TN}))}{k_n \left( \frac{W}{L} \right)_n E_{CL} (V_{DD} - V_{TN})^2}$$

$$\text{for } V_{DD} = 1.8 V :$$

$$\Rightarrow t_{pHL} = C_1 \frac{(E_{CL} + V_{DD} - |V_{TP}|) V_{DD}}{(V_{DD} - |V_{TP}|)^2}$$

$$= \frac{7.78 \times 10^{-12} (1 + 1.8 - 0.7) (1.8)}{(1.8 - 0.7)^2}$$

$$= 24.3 \text{ ps}$$

$$t_{pNL} = \frac{5.71 \times 10^{-12} \times (0.96 + 1.8 - 0.7)}{(1.8 - 0.7)^2} (1.8)$$

$$= 17.49 \text{ ps}$$

$$\approx \boxed{20.1 \text{ ps}}$$

for  $V_{DD} = 1.7V$ ,

$$\Rightarrow t_{PLH} = \frac{2.78 \times 10^{-12} (1 + 1.7 - 0.7)}{(1.7 - 0.7)^2} (1.7)$$

$$= 26.452 \text{ ps}$$

$$t_{PHL} = \frac{5.71 \times 10^{-12} (0.96 + 1.7 - 0.7)}{(1.7 - 0.7)^2} (1.7)$$

$$= 19.02 \text{ ps}$$

$$t_{\text{delay}} = 22.73 \text{ ps} //$$

similarly we can do for other values of  $V_{DD}$  as well.

1.6)

minimally for EDP:

$$① V_{DD} = 1.8V$$

$$EDP = \frac{1}{2} C_{\text{total}} V_{DD}^2 t_p$$

$$= \frac{1}{2} \times 32 \times 10^{-15} \times 1.8^2 \times 20.1 \times 10^{-12}$$

$$= 104.198 \times 10^{-27} = 1.04 \times 10^{-24},$$

$$\text{for } V_{DD} = 1.7V:$$

$$EDP = \frac{1}{2} \times 32 \times 10^{-15} \times 1.7^2 \times 22.73 \times 10^{-12}$$

$$= 105.103 \times 10^{-27}$$



similarly, we can calculate EDP for other values of  $V_{DD}$ .

\* I have made a python script to plot the analytical values & compare it with the simulation values.

\* There is a huge difference in the two, maybe the simulation take the non-idealities into account.

\* but the optimum value for  $V_{DD}$  (EDP optimised) is  $1.4 V_{DD}$

```
import matplotlib.pyplot as plt

vdd_vec = [1.0, 1.1, 1.2, 1.3, 1.4, 1.5, 1.6, 1.7, 1.8]
delayvec_an = []
edpvec_an = []

for vddv in vdd_vec:
    delay_an = 0.5 * (((7.78e-12 * (0.3 + vddv) * vddv) / ((vddv - 0.7)**2)) + ((5.71e-12 * (0.26 + vddv) * vddv) / ((vddv - 0.7)**2)))
    edp_an = 0.5 * 3.2e-15 * vddv**2 * delay_an
    delayvec_an.append(delay_an)
    edpvec_an.append(edp_an)


plt.figure(figsize=(12, 6)) # Adjust figure size as needed

# Plot delayvec_an vs vdd_vec
plt.subplot(1, 2, 1) # Create a subplot (1 row, 2 columns, plot 1)
plt.plot(vdd_vec, delayvec_an)
plt.xlabel('vdd_vec')
plt.ylabel('delayvec_an')
plt.title('delayvec_an vs vdd_vec')
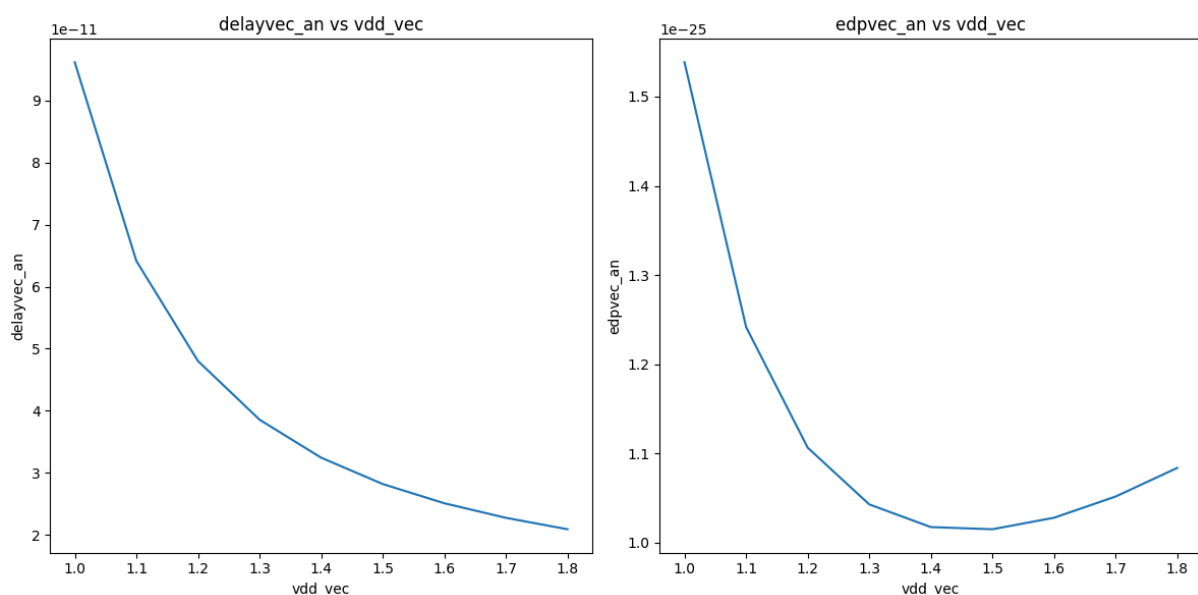
# Plot edpvec_an vs vdd_vec
plt.subplot(1, 2, 2) # Create a subplot (1 row, 2 columns, plot 2)
plt.plot(vdd_vec, edpvec_an)
plt.xlabel('vdd_vec')
plt.ylabel('edpvec_an')
plt.title('edpvec_an vs vdd_vec')


plt.tight_layout() # Adjust spacing between subplots
plt.show() # Display the plots
```

Code for Analytical plotting of delay and edp vs  $V_{DD}$




Analytical Plots for Delay and EDP vs  $V_{DD}$


## Schematic:

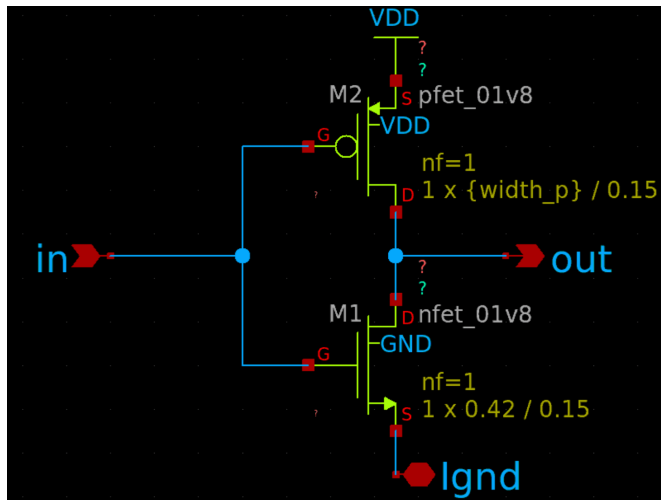

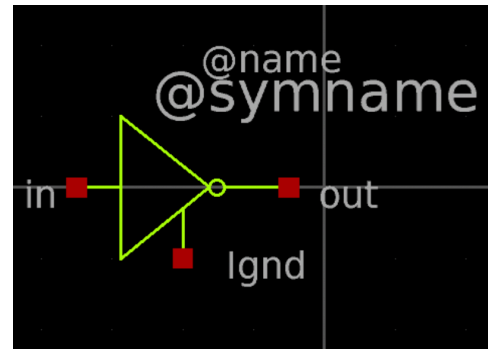Schematic: inverter with parameterized pMOS width with GND input pin



Symbol for inverter given on the left

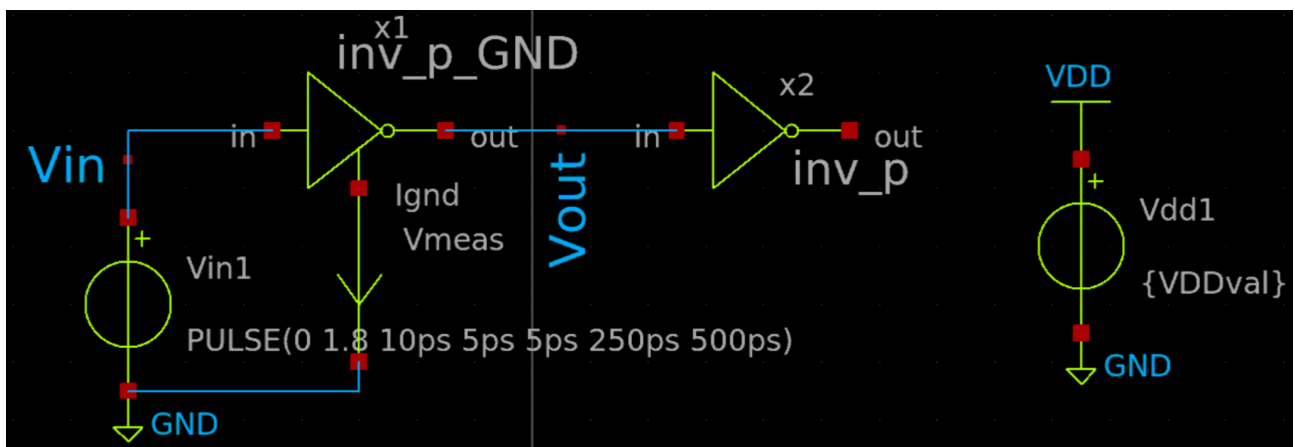


Schematic for 1(b) and 1(c)

## Inference:


From the above observations, we see that the minimum delay is  $W_p = 0.84 \mu\text{m}$  (delay = 19.95 ps).

## Measurements:

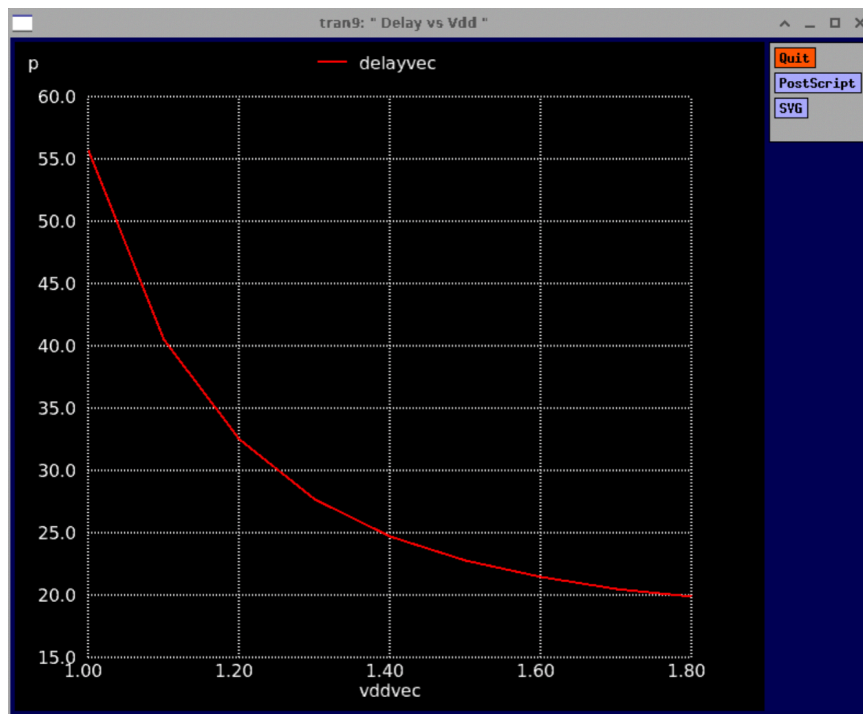

Delay vs  $V_{DD}$

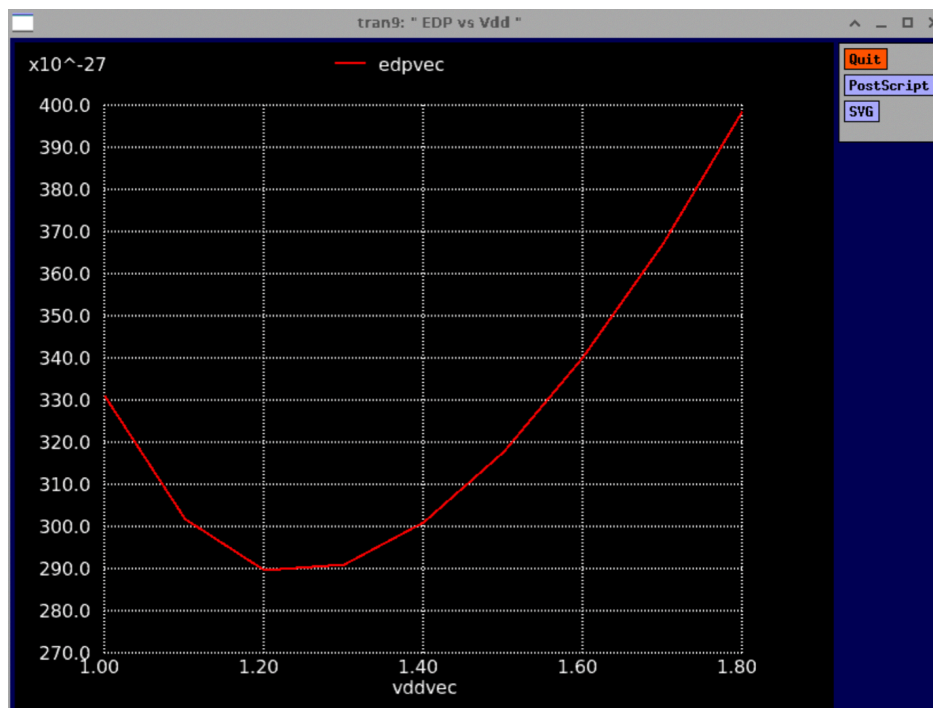- The optimal delay for the given range is at  $V_{DD} = 1.8 \text{ V}$ .



Energy Delay Product (EDP) vs  $V_{DD}$

- The EDP presents a convex nature and the value for  $V_{DD}$  for optimal EDP is  $V_{DD} =$  between 1.2 and 1.3 V., which is very close to the analytical results given above.

## Inference on Delay: 1(b)

so, from  $1.0\text{V} \rightarrow 1.4\text{V}$ , there is a steep decline in delay as in this region:

$$E_{chL} \gg V_{DD} - V_{th}$$

$$\therefore t_{pHL} \propto \frac{V_{DD}}{(V_{DD} - V_{th})^2}$$

$$\propto t_{pHL} \propto \frac{V_{DD}}{(V_{DD} - V_{th})^2}$$

in  $1.4\text{V} \rightarrow 1.8\text{V}$  region, the decline is less steep due to:

$$E_{chL} << V_{DD} - V_{th}$$

$$\therefore t_{pHL} \propto \frac{V_{DD}}{V_{DD} - V_{th}}, \quad t_{pLH} \propto \frac{V_{DD}}{V_{DD} - (V_{th})}$$

## Sim-Code:

```

sim
.param VDDval = 1.8
.param width_p = 0.84
.control
let Nsim = 9
let delayvec = vector(Nsim)
let vddvec = vector(Nsim)
let edpvec = vector(Nsim)
let index = 0
while index < Nsim
    let vddv = 1.0 + (index * 0.1)
    let vby2 = vddv/2
    alterparam VDDval = $vddv
    reset
    tran lp 600p
    meas tran thl trig v(Vin) val = $vby2 rise = 1 targ v(Vout) val = $vby2 fall = 1
    meas tran tlh trig v(Vin) val = $vby2 fall = 1 targ v(Vout) val = $vby2 rise = 1
    meas tran iinteg integ i(vmeas)
    let delayvec[index] = ($&thl + $&tlh)/2
    let vddvec[index] = vddv
    let edpvec[index] = $&iinteg * vddv * delayvec[index]
    let index = index + 1
end
plot delayvec vs vddvec title " Delay vs Vdd "
plot edpvec vs vddvec title " EDP vs Vdd "
print delayvec
.endc

```