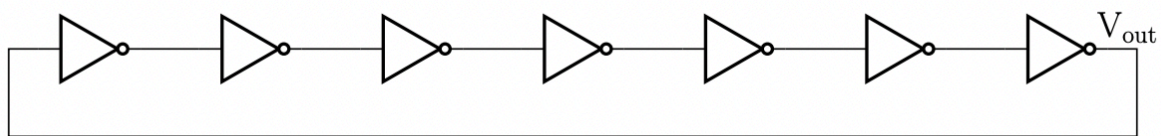


EE5311 Tutorial 4 Report - EE22B070

Himanshu Rajnish Borkar

20/02/2025

1. Construct a seven-stage ring oscillator as shown below and find the oscillating frequency.




1(a) Measure the oscillating frequency for $V_{DD} = 1.8 \text{ V}$

Calculations:


Frequency calculations:

We take the difference of the adjacent rise times when the the $V_{out} = V_{DD}/2$ to get the time period of the waveform, and then reciprocate it to get the waveform's frequency.

Schematic & Code:

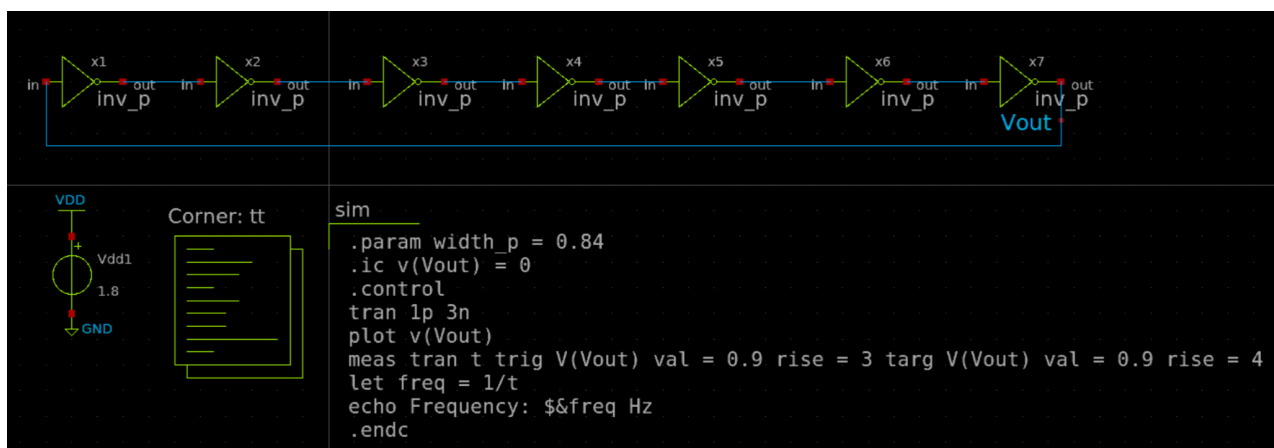

Measurements:

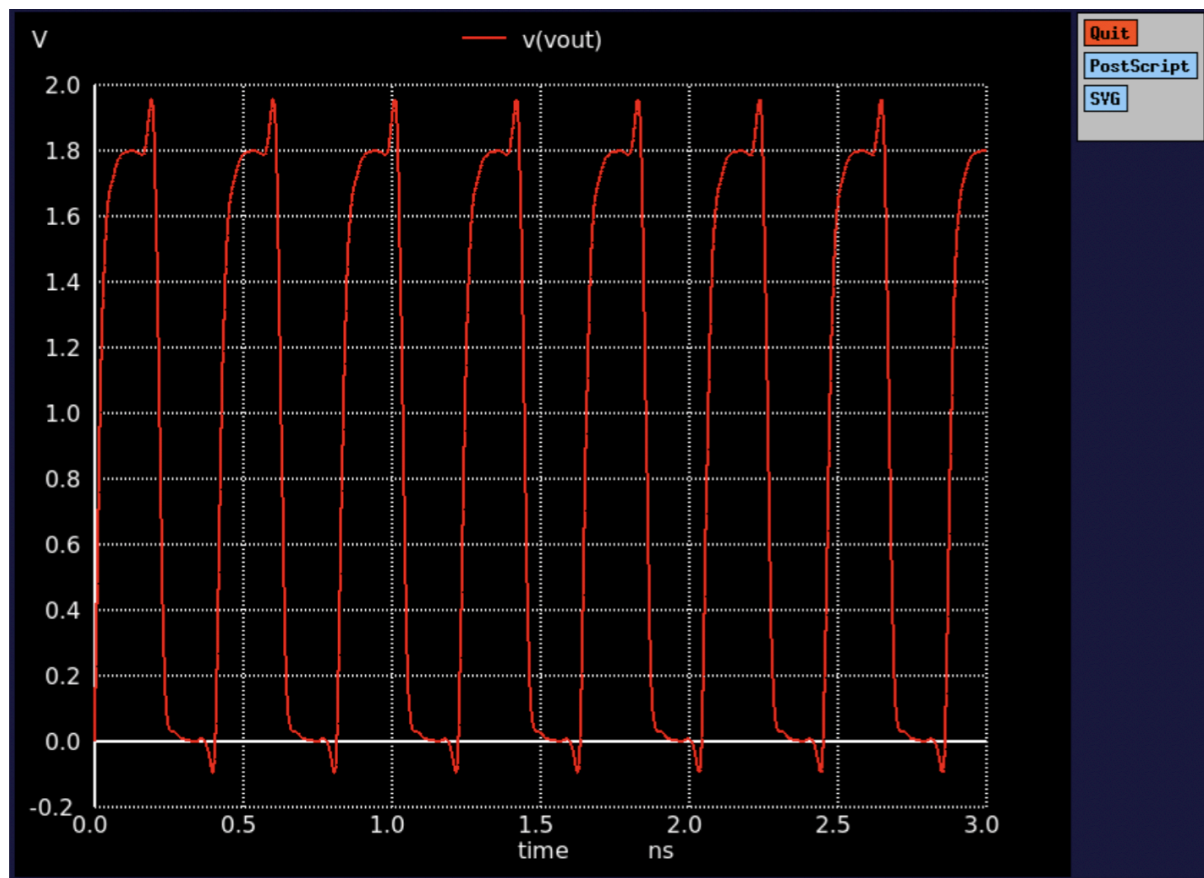

V_{out} vs time gives us a pulse like waveform with spikes


Frequency: 2.44432E+09 Hz
ngspice 2 -> █

From above, we get the frequency to be **2.44 GHz**.

1(b) Plot the oscillating frequency and time period as a function of V_{DD} for $V_{DD} = 1\text{ V}$ to 1.8 V in steps of 0.1 V .

Schematic:

Same as 1(a)

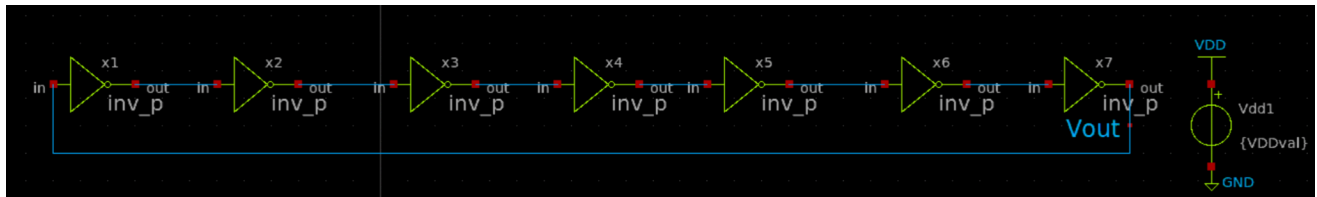


Code:


```
sim
.param width_p = 0.84
.param VDDval = 1.8
.ic V(Vout) = 0
.control
let index = 0
let N = 9
let freq_vec = vector(N)
let vdd_vec = vector(N)

let timeperiod_vec = vector(N)
while index < N
    let vdd = 1.0 + (index * 0.1)
    let vdd_vec[index] = vdd
    let vby2 = vdd/2
    alterparam VDDval = $&vdd
    reset
    tran 1p 10n
    meas tran t trig V(Vout) val = vby2 rise = 3 targ V(Vout) val = vby2 rise = 4
    let freq = 1/t
    let timeperiod_vec[index] = $&t
    let freq_vec[index] = $&freq
    let index = index + 1
    echo Frequency: $&freq Hz
end
print vdd_vec freq_vec
plot freq_vec vs vdd_vec
plot timeperiod_vec vs vdd_vec
.endc
```

Measurements:

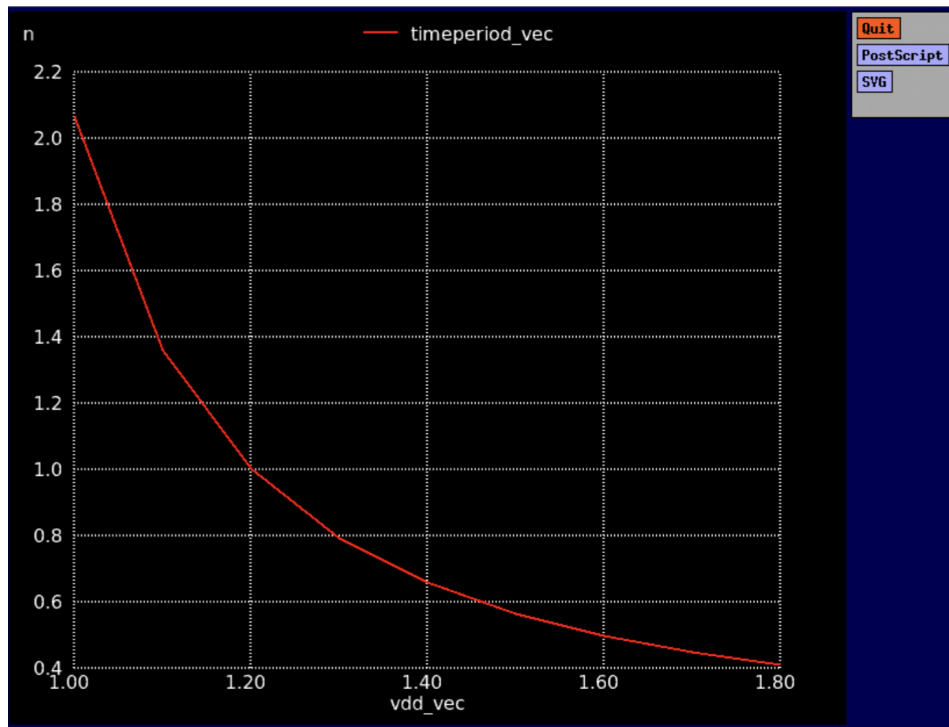

Time period vs V_{DD}

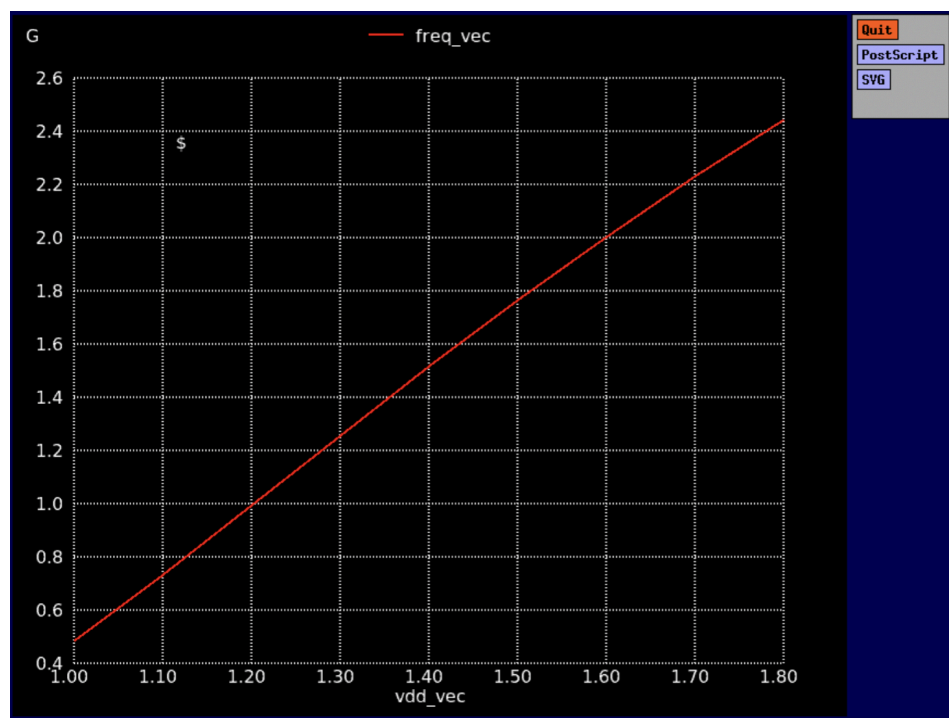


Frequency vs V_{DD}

Index	vdd_vec	freq_vec
0	1.000000e+00	4.842260e+08
1	1.100000e+00	7.338170e+08
2	1.200000e+00	9.955860e+08
3	1.300000e+00	1.258760e+09
4	1.400000e+00	1.517090e+09
5	1.500000e+00	1.766770e+09
6	1.600000e+00	2.005390e+09
7	1.700000e+00	2.231490e+09
8	1.800000e+00	2.444320e+09

Data Points

1(c) Repeat the experiment (b) with nine inverter stages.

Schematic:

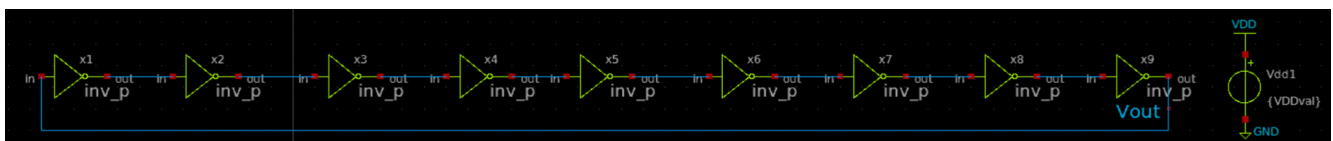


Code:


Same as 1(b)

```
sim
.param width p = 0.84
.param VDDval = 1.8
.ic V(Vout) = 0
.control
let index = 0
let N = 9
let freq_vec = vector(N)
let vdd_vec = vector(N)
let timeperiod_vec = vector(N)
while index < N
    let vdd = 1.0 + (index * 0.1)
    let vdd_vec[index] = vdd
    let vby2 = vdd/2
    alterparam VDDval = $&vdd
    reset
    tran 1p 10n
    meas tran t_trig V(Vout) val = vby2 rise = 3 targ V(Vout) val = vby2 rise = 4
    let freq = 1/t
    let timeperiod_vec[index] = $&t
    let vdd_vec[index] = $&vdd
    let freq_vec[index] = $&freq
    let index = index + 1
    echo Frequency: $&freq Hz
end
print vdd_vec freq_vec
plot freq_vec vs vdd_vec
plot timeperiod_vec vs vdd_vec
.endc
```

Measurements:

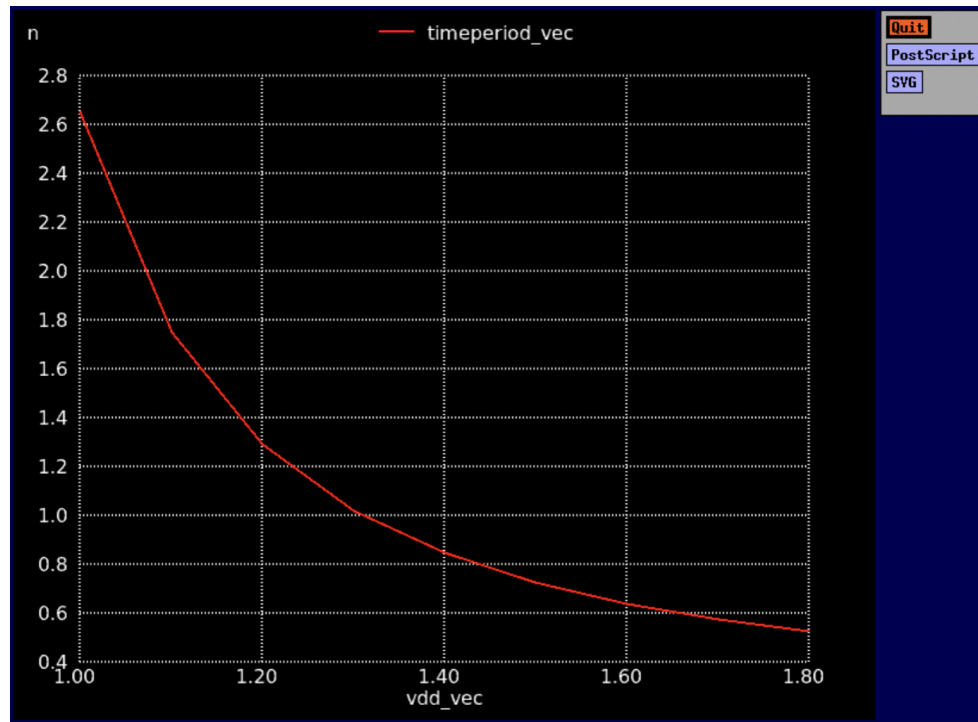

Time period vs V_{DD}

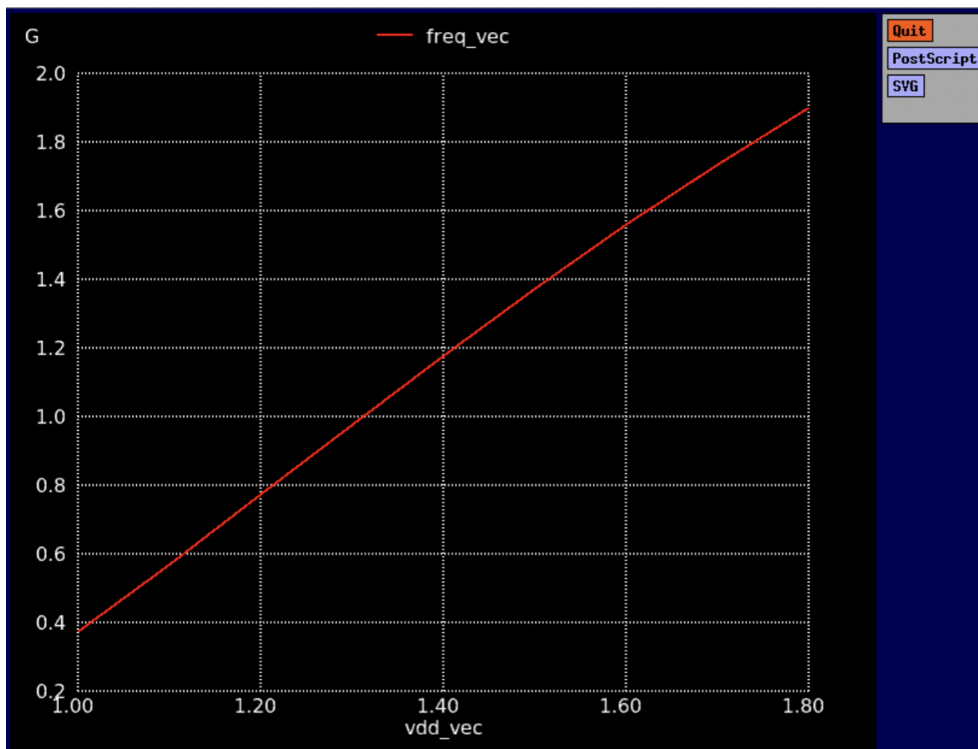

Frequency vs V_{DD}

Index	vdd_vec	freq_vec
0	1.000000e+00	3.766180e+08
1	1.100000e+00	5.707420e+08
2	1.200000e+00	7.743350e+08
3	1.300000e+00	9.790170e+08
4	1.400000e+00	1.179930e+09
5	1.500000e+00	1.374110e+09
6	1.600000e+00	1.559690e+09
7	1.700000e+00	1.735530e+09
8	1.800000e+00	1.901010e+09

Data Points