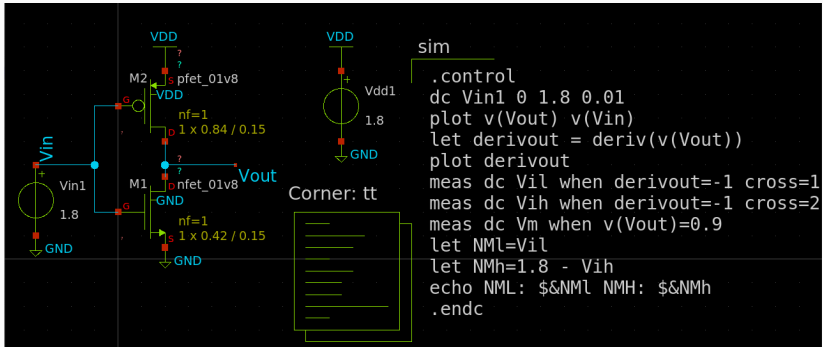


EE5311: Digital IC Design

Tutorial 2

Experiment 2

Plot the derivative and obtain the noise margins:



Experiment 2

Obtain the DC transfer characteristic for V_{DD} ranging from 0.2V to 1.8V in steps of 0.2V.

